

# Digital Design with the Verilog HDL

## Chapter 5 Behavioral Model - part 1

Binh Tran-Thanh

Department of Computer Engineering  
Faculty of Computer Science and Engineering  
Ho Chi Minh City University of Technology

February 28, 2022



# Behavioral Verilog

- Use procedural blocks: **initial**, **always**
- These blocks contain series of statements
  - Abstract – works \*somewhat\* like software
  - Be careful to still remember it's hardware!
- Parallel operation **across** blocks
  - All blocks in a module operate simultaneously
- Sequential **or** parallel operation **within** blocks
  - Depends on the way the block is written
  - Discuss this in a later lecture
- LHS of assignments are **variables**(reg)



# Types of Blocks

## initial

- Behavioral block operates ONCE
- Starts at time 0 (beginning of operation)
- Useful for test benches
- Can sometimes provide initialization of memories/FFs
  - Often better to use "reset" signal
- Inappropriate for combinational logic
- Usually cannot be synthesized

## always

- Behavioral block operates CONTINUOUSLY
- Can use a trigger list to control operation; @(a, b, c)

# initial vs. always

initial

```
reg[7:0] v1, v2, v3, v4;  
initial begin  
    v1 = 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
    #2 v4 = v3 + 1;  
    v1 = v4 + 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
end
```

always

```
reg[7:0] v1, v2, v3, v4;  
always begin  
    v1 = 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
    #2 v4 = v3 + 1;  
    v1 = v4 + 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
end
```

What values does each block produce?



# initial Blocks

```
`timescale 1ns /1ns
module t_full_adder;
  reg [3:0] stim;
  wire s, c;

  // instantiate UUT
  full_adder(sum, carry, stim[2], stim[1], stim[0]);

  // monitor statement is special - only needs to be made once,
  initial $monitor("%t: s=%b c=%b stim=%b", $time, s, c, stim[2:0]);

  // tell our simulation when to stop
  initial #50 $stop;

  initial begin // stimulus generation
    for (stim = 4'd0; stim < 4'd8; stim = stim + 1) begin
      #5;
    end
  end
endmodule
```

*all initial blocks start at time 0*

*single-statement block*

*multi-statement block enclosed by **begin** and **end***



# always Blocks

- Operates continuously or on a trigger list
- Can be used with **initial** blocks
- Cannot "nest" initial or always blocks
- Useful example of continuous always block:

```
reg clock;  
initial clock = 1'b0;  
always #10 clock = ~clock;
```

- Clock generator goes in the **testbench**



# always blocks with trigger lists

- Conditionally "execute" inside of **always** block
  - Always block continuously operating
  - If trigger list present, continuously checking triggers
  - Any change on trigger (sensitivity) list, triggers block

```
always @(a, b, c) begin
    ...
end
```

- Sounds like software! It isn't!
  - This is how the *simulator* treats it
  - The hardware has the same resulting operation, but ...
    - See examples in later slides to see what is **actually** created



# Trigger Lists

- Uses "event control operator" @
- When net or variable in trigger list changes, **always** block is triggered

```
always @(a, b, c) begin
    a1 = a & b;
    a2 = b & c;
    a3 = a & c;
    carry = a1 | a2 | a3;
end
```

```
always @(in1, in0, sel) begin
    if(sel== 1'b0)
        out = in0;
    else
        out = in1;
end
```

```
always @(state, in ) begin
    if(in == 1'b0) begin
        if(state != 2'b11)
            nextstate = state + 1;
        else
            nextstate = 2'b00;
    end
    else
        nextstate = state;
end
```





## Event or

- Original way to specify trigger list `always @ (X1 or X2 or X3)`
- In Verilog 2001 can use , instead of or `always @ (X1, X2, X3)`
- Verilog 2001 also has \* for combinational only `always @(*)`
  - Shortcut that includes all nets/variables used on RHS in statements in the block
  - Also includes variable used in if statements; if (x)
- You may be asked to specify input s to trigger list without \*



## Your turn: comparison module

```
module compare_4bit_behave(  
    output reg A_lt_B, A_gt_B, A_eq_B,  
    input [3:0] A, B);  
  
    always @(A, B) begin  
        .....  
        .....  
        .....  
        .....  
        .....  
        .....  
        .....  
        .....  
    end  
  
endmodule
```

# Edge Triggering

- A negedge is on the transitions
  - $1 \rightarrow x, z, 0$
  - $x, z \rightarrow 0$
- A posedge is on the transitions
  - $0 \rightarrow x, z, 1$
  - $x, z \rightarrow 1$
- Used for clocked (synchronous) logic

```
always @( posedge clk)
    register <= register_input ;
```



## Example: DFF


**Remember** LHS in **always** block is always declared as **reg**.

```
module dff(output reg q, input d, input clk);  
    always @(posedge clk) begin  
        q <= d;  
    end  
endmodule
```

```
module dff_reset(output reg q, input d, clk, reset);  
    always @(posedge clk, negedge reset) begin  
        if(!reset) q <= d;  
        else q <= 0;  
    end  
endmodule
```



# DFF with Set Control

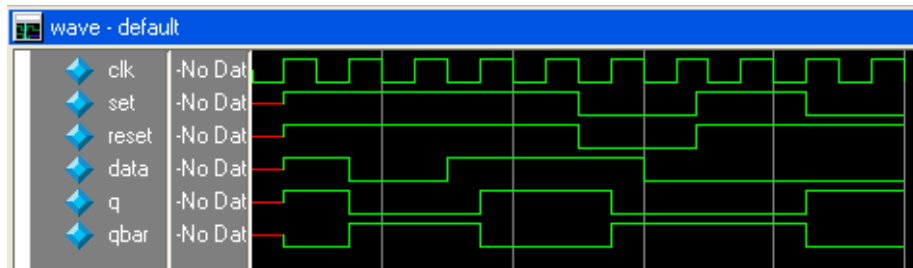

```
module dff(output q, qbar, input reset, set, data, clk);  
    reg ...;  
    always @(posedge clk) begin  
        ...  
    end  
endmodule
```

# Procedural Assignments


- Used within a behavioral block (initial, always)
- Types
  - = *// blocking assignment*
  - <= *// non-blocking assignment*
- Assignments to variables:
  - reg
  - integer
  - real
  - realtime
  - time


 
# Blocking Assignments

- "Evaluated" **sequentially**
- Works a lot like software (**danger!**)
- Used for **combinational** logic


```
module addtree(output reg[9:0] out,  
  input [7:0] in1, in2, in3, in4);  
  reg[8:0] part1, part2;  
  
  always @(in1, in2, in3, in4)  
  begin  
    part1 = in1 + in2;  
    part2 = in3 + in4;  
    out = part1 + part2;  
  end  
endmodule
```


 
# Non-Blocking Assignments

- "Updated" **simultaneously** if no delays given
- Used for **sequential** logic

```
module swap(output reg out0, out1,  
            input rst, clk);  
    always @(posedge clk) begin  
        if(rst) begin  
            out0 <= 1'b0;  
            out1 <= 1'b1;  
        end  
        else begin  
            out0 <= out1;  
            out1 <= out0;  
        end  
    end  
endmodule
```





 
# Swapping

- In blocking, need a "temp" variable

```
module swap(output reg out0, out1,  
            input in0, in1, swap);  
    reg temp;  
  
    always @(*) begin  
        out0 = in0;  
        out1 = in1;  
        if(swap) begin  
            temp = out0;  
            out0 = out1;  
            out1 = temp;  
        end  
    end  
endmodule
```



# Blocking & Non-Blocking Example

```
reg[7:0] A, B, C, D;  
  
always @(posedge clk) begin  
    A = B + C;  
    B = A + D;  
    C = A + B;  
    D = B + D;  
end
```

```
reg[7:0] A, B, C, D;  
  
always @(posedge clk) begin  
    A <= B + C;  
    B <= A + D;  
    C <= A + B;  
    D <= B + D;  
end
```

- Assume initially that  $A = 1$ ,  $B = 2$ ,  $C = 3$ , and  $D = 4$
- Note: shouldn't use blocking with sequential!



# Correcting The Example

```
reg[7:0] A, B, C, D;  
reg[7:0] newA, newB, newC, newD;
```

```
always @(posedge clk) begin  
    A <= newA; B <= newB;  
    C <= newC; D <= newD;  
end
```

```
always @(*) begin  
    newA = B + C;  
    newB = newA + D;  
    newC = newA + newB;  
    newD = newB + D;  
end
```

```
reg[7:0] A, B, C, D;
```

```
always @(posedge clk)  
    begin  
        A <= B + C;  
        B <= B + C + D;  
        C <= B + C + B + C + D;  
        D <= B + C + D + D;  
    end
```



# Why Not '=' In Sequential?

Yes, it can "work", but...

- $\leq$  models pipeline stages better
- $=$  can cause problems if multiple always blocks
- Order of statements is important with  $=$

Use the style guidelines given!

- $\leq$  for sequential block
- $=$  for combinational block
- Don't mix in same block!




# Shift Register: Blocking


```
module shiftreg(A, E, clk, rst);  
    output A;  
    input E, clk, rst;  
    reg A, B, C, D;  
    always @ (posedge clk or posedge rst) begin  
        if(rst) begin A = 0; B = 0; C = 0; D = 0; end  
        else begin A = B; B = C; C = D; D = E;  
            end// option 1  
  
        //else begin D = E; C = D; B = C; A = B;  
        //end// option 2  
    end  
endmodule
```

- What do we get with each option?

# Shift Register: Blocking

 

The order is matters!

 

# Combinational vs. Sequential

## Combinational

- Not edge-triggered
- All "input s" (RHS nets/variables) are triggers
- Does not depend on clock

## Sequential

- Edge-triggered by clock signal
- Only clock (and possibly reset) appear in trigger list
- Can include combinational logic that feeds a FF or register

